

# 11 Logic Gates Test

Your Name: \_\_\_\_\_

AND	NAND	OR	NOR	XOR	NOT																																																																	
$\begin{matrix} A \\ B \end{matrix} \quad \neg Q$ $Q = A \quad B$	$\begin{matrix} A \\ B \end{matrix} \quad \neg Q$ $Q = A \quad B$	$\begin{matrix} A \\ B \end{matrix} \quad \neg Q$ $Q = A \quad B$	$\begin{matrix} A \\ B \end{matrix} \quad \neg Q$ $Q = A \quad B$	$\begin{matrix} A \\ B \end{matrix} \quad \neg Q$ $Q = A \quad B$	$A \quad \neg Q$ $Q =$																																																																	
Two ones give a Anything else gives	Two ones give a Anything else gives	Two zeros give a Anything else gives	Two zeros give a Anything else gives	Equal inputs give a Anything else gives	Input is																																																																	
<table border="1"> <thead> <tr><th>A</th><th>B</th><th>Q</th></tr> </thead> <tbody> <tr><td>0</td><td>0</td><td></td></tr> <tr><td>0</td><td>1</td><td></td></tr> <tr><td>1</td><td>0</td><td></td></tr> <tr><td>1</td><td>1</td><td></td></tr> </tbody> </table>	A	B	Q	0	0		0	1		1	0		1	1		<table border="1"> <thead> <tr><th>A</th><th>B</th><th>Q</th></tr> </thead> <tbody> <tr><td>0</td><td>0</td><td></td></tr> <tr><td>0</td><td>1</td><td></td></tr> <tr><td>1</td><td>0</td><td></td></tr> <tr><td>1</td><td>1</td><td></td></tr> </tbody> </table>	A	B	Q	0	0		0	1		1	0		1	1		<table border="1"> <thead> <tr><th>A</th><th>B</th><th>Q</th></tr> </thead> <tbody> <tr><td>0</td><td>0</td><td></td></tr> <tr><td>0</td><td>1</td><td></td></tr> <tr><td>1</td><td>0</td><td></td></tr> <tr><td>1</td><td>1</td><td></td></tr> </tbody> </table>	A	B	Q	0	0		0	1		1	0		1	1		<table border="1"> <thead> <tr><th>A</th><th>B</th><th>Q</th></tr> </thead> <tbody> <tr><td>0</td><td>0</td><td></td></tr> <tr><td>0</td><td>1</td><td></td></tr> <tr><td>1</td><td>0</td><td></td></tr> <tr><td>1</td><td>1</td><td></td></tr> </tbody> </table>	A	B	Q	0	0		0	1		1	0		1	1		<table border="1"> <thead> <tr><th>A</th><th>Q</th></tr> </thead> <tbody> <tr><td>0</td><td></td></tr> <tr><td>1</td><td></td></tr> </tbody> </table>	A	Q	0		1	
A	B	Q																																																																				
0	0																																																																					
0	1																																																																					
1	0																																																																					
1	1																																																																					
A	B	Q																																																																				
0	0																																																																					
0	1																																																																					
1	0																																																																					
1	1																																																																					
A	B	Q																																																																				
0	0																																																																					
0	1																																																																					
1	0																																																																					
1	1																																																																					
A	B	Q																																																																				
0	0																																																																					
0	1																																																																					
1	0																																																																					
1	1																																																																					
A	Q																																																																					
0																																																																						
1																																																																						
<table border="1"> <thead> <tr><th>B \ A</th><th>0</th><th>1</th></tr> </thead> <tbody> <tr><th>0</th><td></td><td></td></tr> <tr><th>1</th><td></td><td></td></tr> </tbody> </table>	B \ A	0	1	0			1			<table border="1"> <thead> <tr><th>B \ A</th><th>0</th><th>1</th></tr> </thead> <tbody> <tr><th>0</th><td></td><td></td></tr> <tr><th>1</th><td></td><td></td></tr> </tbody> </table>	B \ A	0	1	0			1			<table border="1"> <thead> <tr><th>B \ A</th><th>0</th><th>1</th></tr> </thead> <tbody> <tr><th>0</th><td></td><td></td></tr> <tr><th>1</th><td></td><td></td></tr> </tbody> </table>	B \ A	0	1	0			1			<table border="1"> <thead> <tr><th>B \ A</th><th>0</th><th>1</th></tr> </thead> <tbody> <tr><th>0</th><td></td><td>1</td></tr> <tr><th>1</th><td>1</td><td></td></tr> </tbody> </table>	B \ A	0	1	0		1	1	1		<table border="1"> <thead> <tr><th>A</th><th>0</th><th>1</th></tr> </thead> <tbody> <tr><th>Q</th><td></td><td></td></tr> </tbody> </table>	A	0	1	Q																										
B \ A	0	1																																																																				
0																																																																						
1																																																																						
B \ A	0	1																																																																				
0																																																																						
1																																																																						
B \ A	0	1																																																																				
0																																																																						
1																																																																						
B \ A	0	1																																																																				
0		1																																																																				
1	1																																																																					
A	0	1																																																																				
Q																																																																						

1. In the diagram above, fill in all the missing bits ...

- Six logic gate symbols.
- Six Boolean expressions with missing operators.
- Six one-sentence rules.
- Six conventional truth tables.
- Six alternative truth tables.